

# Lab 9-10 – Nano Processor Design Competition

## CS1050 Computer Organization and Digital Design

### Group 100:

- 210296X – Kopimenan L.
- 210554M – Sajeev K.

### Lab Task:

Designing a simple nano processor which can execute the below assembly instructions.

1. ADD (Addition)
2. MOV (Move)
3. NEG (Negation) 2's complement
4. JZR (Jump) Jump to an instruction if condition is met.

The following components were asked to build and then they were

1. 4-bit Add/Subtract unit
2. 3-bit adder
3. 3-bit Program Counter (PC)
4. k-way b-bit multiplexers
5. Register Bank
6. Program ROM
7. Instruction Decoder

calculating the total between 1 to 3 and simulating the addition of 1,2 and 3 and load it to R7(8th register) were the tasks that the Program Rom contains and executes by the processor. Program contains these tasks as hard coded assembly language instructions.

ASSEMBLY CODE	MACHINE CODE REPRESENTATION
---------------	-----------------------------

MOV R7,0	101110000000
MOV R1,1	100010000001
MOV R2,2	100100000010
MOV R3,3	100110000011
ADD R7,R1	001110010000
ADD R7,R2	001110100000
ADD R7,R3	001110110000
JZR R3,0	110110000000

Testing and verifying the functionality of the nano processor on the Basys 3 should be done.

## VHDL codes

### Half Adder

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity MUX_8_way_4_Bit is
```

```
    Port ( R0 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          R1 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          R2 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          R3 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          R4 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          R5 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          R6 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          R7 : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          S : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          Q : out STD_LOGIC_VECTOR (3 downto 0));
```

```
end MUX_8_way_4_Bit;
```

```
architecture Behavioral of MUX_8_way_4_Bit is
```

```
begin
```

```
    process(R0,R1,R2,R3,R4,R5,R6,R7,S)
```

```
    begin
```

```
        case S is
```

```
            when "000" => Q <= R0;
```

```
            when "001" => Q <= R1;
```

```
            when "010" => Q <= R2;
```

```
            when "011" => Q <= R3;
```

```
            when "100" => Q <= R4;
```

```
            when "101" => Q <= R5;
```

```
            when "110" => Q <= R6;
```

```
            when "111" => Q <= R7;
```

```
        when others => Q <= "ZZZZ";

    end case;

end process;

end Behavioral;
```

### **Full Adder**

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity FA is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          C_in : in STD_LOGIC;
          S : out STD_LOGIC;
          C_out : out STD_LOGIC);
end FA;

architecture Behavioral of FA is
    component HA
        port(
            A : in std_logic;
            B : in std_logic;
            C : out std_logic;
            S : out std_logic);
```

```

end component;

SIGNAL HA0_S, HA0_C, HA1_S, HA1_C : std_logic;

begin

  HA_0 : HA
    port map (
      A => A,
      B => B,
      S => HA0_S,
      C => HA0_C);

  HA_1 : HA
    port map (
      A => HA0_S,
      B => C_in,
      S => HA1_S,
      C => HA1_C);

  S <= HA1_S;

  C_out <= HA0_C OR HA1_C;

end Behavioral;

```

### **Registrer**

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity Reg is
  Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
        En : in STD_LOGIC;
        Clk : in STD_LOGIC;
        Reset : in STD_LOGIC;
        Q : out STD_LOGIC_VECTOR (3 downto 0));
end Reg;

```

architecture Behavioral of Reg is

```

begin
process(Clk, Reset)
begin
    if(Reset ='1') then
        Q<="0000";
    elsif(rising_edge(Clk)) then

        if(En = '1') then
            Q <= D;
        end if;
    end if;
end process;
end Behavioral;

```

#### **4bit Ripple Carry Adder**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity RCA_4 is
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          S : out STD_LOGIC_VECTOR (3 downto 0);
          C_in : in STD_LOGIC;
          C_out : out STD_LOGIC );
end RCA_4;

architecture Behavioral of RCA_4 is
    component FA
        Port ( A : in STD_LOGIC;
              B : in STD_LOGIC;
              C_in : in STD_LOGIC;
              S : out STD_LOGIC;
              C_out : out STD_LOGIC);
    end component FA

```

```
end component;
```

```
signal FA0_S, FA0_C, FA1_S, FA1_C, FA2_S, FA2_C, FA3_S, FA3_C : STD_LOGIC;
```

```
begin
```

```
    FA_0 : FA
```

```
        port map (
```

```
            A => A(0),
```

```
            B => B(0),
```

```
            C_in => C_in,
```

```
            S => S(0),
```

```
            C_Out => FA0_C);
```

```
    FA_1 : FA
```

```
        port map (
```

```
            A => A(1),
```

```
            B => B(1),
```

```
            C_in => FA0_C,
```

```
            S => S(1),
```

```
            C_Out => FA1_C);
```

```
    FA_2 : FA
```

```
        port map (
```

```
            A => A(2),
```

```
            B => B(2),
```

```
            C_in => FA1_C,
```

```
            S => S(2),
```

```
            C_Out => FA2_C);
```

```
    FA_3 : FA
```

```
        port map (
```

```
            A => A(3),
```

```
            B => B(3),
```

```
            C_in => FA2_C,
```

```
S => S(3),  
C_Out => C_out);
```

```
end Behavioral;
```

### **Lookup table for 7 segment display**

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.NUMERIC_STD.ALL;
```

```
entity LUT_16_7 is
```

```
    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
```

```
          data : out STD_LOGIC_VECTOR (6 downto 0));
```

```
end LUT_16_7;
```

```
architecture Behavioral of LUT_16_7 is
```

```
    type rom_type is array (0 to 15) of std_logic_vector(6 downto 0);
```

```
    signal sevenSegment_ROM : rom_type := (
```

```
        "0000001", -- 0
```

```
        "1001111", --1
```

```
        "0010010", --2
```

```
        "0000110", --3
```

```
        "1001100", --4
```

```
        "0100100", --5
```

```
        "0100000", --6
```

```
        "0001111", --7
```

```
        "0000000", --8
```

```
        "0000100", --9
```

```
        "0001000", -- a
```

```
        "1100000", --b
```

```
        "0110001", --c
```

```

    "1000010", --d
    "0110000", --e
    "0111000" -- f
);
begin
data <= sevenSegment_ROM(to_integer(unsigned(address)));
end Behavioral;

```

### **Decoder 3 to 8**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Decoder_3_to_8 is
    Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
          EN : in STD_LOGIC := '1';
          Y : out STD_LOGIC_VECTOR (7 downto 0));
end Decoder_3_to_8;

```

architecture Behavioral of Decoder\_3\_to\_8 is

```

begin

process (I)
begin
if I = "000" then
    Y <= "00000001";
elsif I = "001" then
    Y <= "00000010";
elsif I = "010" then
    Y <= "00000100";
elsif I = "011" then
    Y <= "00001000";
elsif I = "100" then

```



```

        Y <= "00010000";
    elsif I = "101" then
        Y <= "00100000";
    elsif I = "110" then
        Y <= "01000000";
    else
        Y <= "10000000";
    end if;
end process;

end Behavioral;

```

## **Muxes**

### **2way 3bit**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity MUX_2_way_3_Bit is
    Port ( I0 : in STD_LOGIC_VECTOR (2 downto 0);
          I1 : in STD_LOGIC_VECTOR (2 downto 0);
          S : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (2 downto 0));
end MUX_2_way_3_Bit;

architecture Behavioral of MUX_2_way_3_Bit is

begin
    process(I0,I1,S)
    begin
        case S is
            when '0' => Q <= I0;

```

```
        when '1' => Q <= I1;

        when others => Q <= "ZZZ";

    end case;

end process;

end Behavioral;
```

## **2way 4bit**

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;
```

```
entity MUX_2_way_4_Bit is
    Port ( Adder_Sub_Out : in STD_LOGIC_VECTOR (3 downto 0);
          Imd_Value : in STD_LOGIC_VECTOR (3 downto 0);
          S : in STD_LOGIC;
          Q : out STD_LOGIC_VECTOR (3 downto 0));
end MUX_2_way_4_Bit;
```

```
architecture Behavioral of MUX_2_way_4_Bit is
```

```
begin

    process(Adder_Sub_Out, Imd_Value, S)
    begin
        case S is
            when '0' => Q <= Adder_Sub_Out ;
            when '1' => Q <= Imd_Value ;
            when others => Q <= "ZZZZ";
        end case;
    end process;

end Behavioral;
```

## **8way 4bit**

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity MUX\_8\_way\_4\_Bit is

Port ( R0 : in STD\_LOGIC\_VECTOR (3 downto 0);

      R1 : in STD\_LOGIC\_VECTOR (3 downto 0);

      R2 : in STD\_LOGIC\_VECTOR (3 downto 0);

      R3 : in STD\_LOGIC\_VECTOR (3 downto 0);

      R4 : in STD\_LOGIC\_VECTOR (3 downto 0);

      R5 : in STD\_LOGIC\_VECTOR (3 downto 0);

      R6 : in STD\_LOGIC\_VECTOR (3 downto 0);

      R7 : in STD\_LOGIC\_VECTOR (3 downto 0);

      S : in STD\_LOGIC\_VECTOR (2 downto 0);

      Q : out STD\_LOGIC\_VECTOR (3 downto 0));

end MUX\_8\_way\_4\_Bit;

architecture Behavioral of MUX\_8\_way\_4\_Bit is

begin

  process(R0,R1,R2,R3,R4,R5,R6,R7,S)

  begin

    case S is

      when "000" => Q <= R0;

      when "001" => Q <= R1;

      when "010" => Q <= R2;

      when "011" => Q <= R3;

      when "100" => Q <= R4;

      when "101" => Q <= R5;

      when "110" => Q <= R6;

      when "111" => Q <= R7;

      when others => Q <= "ZZZZ";

    end case;

```
end process;  
end Behavioral;
```

## **Program Rom**

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.NUMERIC_STD.ALL;
```

```
entity Program_Rom is  
    Port ( address : in STD_LOGIC_VECTOR (2 downto 0);  
          data : out STD_LOGIC_VECTOR (11 downto 0));  
end Program_Rom;
```

```
architecture Behavioral of Program_Rom is
```

```
type rom_type is array (0 to 7) of std_logic_vector(11 downto 0);
```

```
signal program_ROM : rom_type := (
```

```
    "101110000000", -- MOVI R7, 0
```

```
    "101100000001", -- MOVI R6, 1
```

```
    "101010000010", -- MOVI R5, 2
```

```
    "101000000011", -- MOVI R4, 3
```

```
    "001111100000", -- ADD R7, R6
```

```
    "001111010000", -- ADD R7, R5
```

```
    "001111000000", -- ADD R7, R4
```

```
    "110110000000" -- JZR R3, 0
```

```
);
```

```
begin
```

```
data <= program_ROM(to_integer(unsigned(address)));
```

```
end Behavioral;
```

## **Slowclock for xsim simulation**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Slow_Clk is
    Port ( Clk_in : in STD_LOGIC;
          Clk_out : out STD_LOGIC);
end Slow_Clk;

architecture Behavioral of Slow_Clk is

    signal count : integer := 1;
    signal clk_status : std_logic := '0';

begin
    process (Clk_in) begin
        if (rising_edge(Clk_in)) then
            count <= count + 1;
            if (count = 1) then
                clk_status <= not clk_status;
                Clk_out <= clk_status;
                count <= 1;
            end if;
        end if;
    end process;

end Behavioral;
```

## **Program counter**

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity Program\_Counter is

Port ( D : in STD\_LOGIC\_VECTOR (2 downto 0);

En : in STD\_LOGIC;

Reset : in STD\_LOGIC;

Clk : in STD\_LOGIC;

Q : out STD\_LOGIC\_VECTOR (2 downto 0));

end Program\_Counter;

architecture Behavioral of Program\_Counter is

begin

process (Clk, Reset) begin

if (rising\_edge(Clk)) then

if (Reset = '0') then

if (NOT(D="000")) then

Q <= D;

end if;

else

Q <= "000";

end if;

end if;

end process;

end Behavioral;

## **Register bank**

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity Register\_Bank is

Port ( Reg\_en : in STD\_LOGIC\_VECTOR (2 downto 0);

Clk : in STD\_LOGIC;

Reset : in STD\_LOGIC;

Inp : in STD\_LOGIC\_VECTOR (3 downto 0);

Q0 : out STD\_LOGIC\_VECTOR (3 downto 0);

Q1 : out STD\_LOGIC\_VECTOR (3 downto 0);

Q2 : out STD\_LOGIC\_VECTOR (3 downto 0);

Q3 : out STD\_LOGIC\_VECTOR (3 downto 0);

Q4 : out STD\_LOGIC\_VECTOR (3 downto 0);

Q5 : out STD\_LOGIC\_VECTOR (3 downto 0);

Q6 : out STD\_LOGIC\_VECTOR (3 downto 0);

Q7 : out STD\_LOGIC\_VECTOR (3 downto 0));

end Register\_Bank;

architecture Behavioral of Register\_Bank is

component Decoder\_3\_to\_8

Port ( I : in STD\_LOGIC\_VECTOR (2 downto 0);

EN : in STD\_LOGIC;

Y : out STD\_LOGIC\_VECTOR (7 downto 0));

end component;

component Reg

Port ( D : in STD\_LOGIC\_VECTOR (3 downto 0);

En : in STD\_LOGIC;

Clk : in STD\_LOGIC;

Reset : in STD\_LOGIC;

Q : out STD\_LOGIC\_VECTOR (3 downto 0));

```
end component;
```

```
SIGNAL Y : STD_LOGIC_VECTOR (7 downto 0);
```

```
begin
```

```
Decoder_3_to_8_0: Decoder_3_to_8
```

```
PORT MAP(
```

```
    I=>Reg_en,
```

```
    EN =>'1',
```

```
    Y=>Y);
```

```
R0 : Reg
```

```
PORT MAP(
```

```
    D=>"0000",
```

```
    En => '0',
```

```
    Clk => Clk,
```

```
    Reset => Reset,
```

```
    Q=> Q0 );
```

```
R1 : Reg
```

```
PORT MAP(
```

```
    D=>Inp,
```

```
    En => Y(1),
```

```
    Clk => Clk,
```

```
    Reset => Reset,
```

```
    Q=> Q1);
```

```
R2 : Reg
```

```
PORT MAP(
```

```
    D=>Inp,
```

```
    En => Y(2),
```

```
    Clk => Clk,
```

```
    Reset => Reset,
```

```
    Q=> Q2);
```



R3 : Reg

PORT MAP(

D=>Inp,

En => Y(3),

Clk => Clk,

Reset => Reset,

Q=> Q3);

R4 : Reg

PORT MAP(

D=>Inp,

En => Y(4),

Clk => Clk,

Reset => Reset,

Q=> Q4);

R5 : Reg

PORT MAP(

D=>Inp,

En => Y(5),

Clk => Clk,

Reset => Reset,

Q=> Q5);

R6 : Reg

PORT MAP(

D=>Inp,

En => Y(6),

Clk => Clk,

Reset => Reset,

Q=> Q6);

R7 : Reg

PORT MAP(

```
D=>Inp,  
En => Y(7),  
Clk => Clk,  
Reset => Reset,  
Q=> Q7);  
end Behavioral;
```

## **Adder Sub**

```
library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity Add_Sub_Unit is
```

```
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);  
          B : in STD_LOGIC_VECTOR (3 downto 0);  
          Sel : in STD_LOGIC; -- Add/Sub Selector --sel=0 ADD , sel=1 SUBSTRACT  
          S : out STD_LOGIC_VECTOR (3 downto 0);  
          C_Out : out STD_LOGIC; -- Carry flag  
          Z_Out : out STD_LOGIC; -- Zero flag  
          N_Out : out STD_LOGIC; -- Negetive flag  
          P_Out : out STD_LOGIC );-- Parity flag (Odd parity detector)
```

```
end Add_Sub_Unit;
```

```
architecture Behavioral of Add_Sub_Unit is
```

```
    component RCA_4
```

```
        Port ( A : in STD_LOGIC_VECTOR (3 downto 0);  
              B : in STD_LOGIC_VECTOR (3 downto 0);  
              S : out STD_LOGIC_VECTOR (3 downto 0);  
              C_in : in STD_LOGIC;  
              C_out : out STD_LOGIC );
```

```
end component;
```

```
signal B_Sel, S_out : STD_LOGIC_VECTOR (3 downto 0);
```

```

begin

B_Sel(0) <= B(0) XOR Sel;

B_Sel(1) <= B(1) XOR Sel;

B_Sel(2) <= B(2) XOR Sel;

B_Sel(3) <= B(3) XOR Sel;


RCA_4_0 : RCA_4
  port map (
    B => B_Sel,
    A => A,
    C_in => Sel,
    S => S_out,
    C_Out => C_Out);


S <= S_out;

Z_Out <= NOT (S_out(0) OR S_out(1) OR S_out(2) OR S_out(3));

N_Out <= S_out(3);

P_Out <= S_out(0) XOR S_out(1) XOR S_out(2) XOR S_out(3);


end Behavioral;

```

## **Instruction decoder**

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;


entity Instuction_Decoder is

  Port ( Instruction : in STD_LOGIC_VECTOR (11 downto 0);

        Reg_en : out STD_LOGIC_VECTOR (2 downto 0);

        Load_sel : out STD_LOGIC;

        lmd_Val : out STD_LOGIC_VECTOR (3 downto 0);

        Reg_SelA : out STD_LOGIC_VECTOR (2 downto 0);

        Reg_SelB : out STD_LOGIC_VECTOR (2 downto 0);

        Add_SubSel : out STD_LOGIC;

```

```
Jump_add : out STD_LOGIC_VECTOR (2 downto 0);  
Jump_flag : out STD_LOGIC;  
Reg_Check_Jmp : in STD_LOGIC_VECTOR (3 downto 0));
```

```
end Instuction_Decoder;
```

architecture Behavioral of Instuction\_Decoder is

```
begin
```

```
process(Instruction, Reg_Check_Jmp)
```

```
begin
```

```
Reg_en <= "000";
```

```
Load_sel <= '0';
```

```
Imd_Val <= "0000";
```

```
Reg_SelA <= "000";
```

```
Reg_SelB <= "000";
```

```
Add_SubSel <= '0';
```

```
Jump_add <= "000";
```

```
Jump_flag <= '0';
```

```
If (Instruction(11)='0' and Instruction(10)='0') then
```

```
Reg_en<= Instruction (9 downto 7);
```

```
Load_sel <= '0';
```

```
Reg_SelA <= Instruction (9 downto 7);
```

```
Reg_SelB <= Instruction (6 downto 4);
```

```
Add_SubSel <= '0';
```

```
elsif (Instruction(11)='0' and Instruction(10)='1') then
```

```
Reg_en <= Instruction(9 downto 7);
```

```
Load_sel <= '0';
```

```
Reg_SelA <= "000";
```

```
Reg_SelB <= Instruction (9 downto 7);
```

```
Add_SubSel <= '1';
```

```

elsif (Instruction(11)='1' and Instruction(10)='0') then
    Reg_en <= Instruction(9 downto 7);
    Load_sel <= '1';
    lmd_Val <= Instruction(3 downto 0);
elsif (Instruction(11)='1' and Instruction(10)='1') then
    Reg_en <= "000";
    Reg_SelA <= Instruction (9 downto 7);
    if (Reg_Check_Jmp = "0000") then
        Jump_flag <= '1';
        Jump_add <= Instruction(2 downto 0);
    else
        Jump_flag <= '0';
    end if;
end if;
end if;

```

### **3bit Adder**

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Adder_3_Bit is
    Port ( A : in STD_LOGIC_VECTOR (2 downto 0);
          C_in : in STD_LOGIC;
          S : out STD_LOGIC_VECTOR (2 downto 0);
          C_out : out STD_LOGIC);
end Adder_3_Bit;

architecture Behavioral of Adder_3_Bit is

    component FA
        port(
            A : in std_logic;
            B : in std_logic;

```

```
C_in : in std_logic;  
S : out std_logic;  
C_out : out std_logic);  
end component;
```

```
SIGNAL FA0_S, FA0_C, FA1_S, FA1_C, FA2_S : std_logic;  
SIGNAL B : STD_LOGIC_VECTOR (2 downto 0) := "001";
```

```
begin
```

```
FA_0 : FA
```

```
    port map (  
        A => A(0),  
        B => B(0),  
        C_in => '0',  
        S => S(0),  
        C_out => FA0_C);
```

```
FA_1 : FA
```

```
    port map (  
        A => A(1),  
        B => B(1),  
        C_in => FA0_C,  
        S => S(1),  
        C_out => FA1_C);
```

```
FA_2 : FA
```

```
    port map (  
        A => A(2),  
        B => B(2),  
        C_in => FA1_C,  
        S => S(2),  
        C_out => C_out);
```

end Behavioral;

## **Nano Processor**

library IEEE;

use IEEE.STD\_LOGIC\_1164.ALL;

entity NanoProcessor is

```
Port ( Clk : in STD_LOGIC;
      Reset : in STD_LOGIC;
      Overflow : out STD_LOGIC;
      Zero : out STD_LOGIC;
      R7 : out STD_LOGIC_VECTOR (3 downto 0);
      seg7_out : out STD_LOGIC_VECTOR (6 downto 0);
      anode : out STD_LOGIC_VECTOR (3 downto 0)
    );
```

end NanoProcessor;

architecture Behavioral of NanoProcessor is

component LUT\_16\_7

```
Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
      data : out STD_LOGIC_VECTOR (6 downto 0));
```

end component;

component Slow\_Clk

```
Port ( Clk_in : in STD_LOGIC;
      Clk_out : out STD_LOGIC);
```

end component;

component Register\_Bank

Port ( Reg\_en : in STD\_LOGIC\_VECTOR (2 downto 0);

Clk : in STD\_LOGIC;

Reset : in STD\_LOGIC;

Inp : in STD\_LOGIC\_VECTOR (3 downto 0);

Q0 : out STD\_LOGIC\_VECTOR (3 downto 0);

Q1 : out STD\_LOGIC\_VECTOR (3 downto 0);

Q2 : out STD\_LOGIC\_VECTOR (3 downto 0);

Q3 : out STD\_LOGIC\_VECTOR (3 downto 0);

Q4 : out STD\_LOGIC\_VECTOR (3 downto 0);

Q5 : out STD\_LOGIC\_VECTOR (3 downto 0);

Q6 : out STD\_LOGIC\_VECTOR (3 downto 0);

Q7 : out STD\_LOGIC\_VECTOR (3 downto 0));

end component;

component MUX\_8\_way\_4\_Bit

Port ( R0 : in STD\_LOGIC\_VECTOR (3 downto 0);

R1 : in STD\_LOGIC\_VECTOR (3 downto 0);

R2 : in STD\_LOGIC\_VECTOR (3 downto 0);

R3 : in STD\_LOGIC\_VECTOR (3 downto 0);

R4 : in STD\_LOGIC\_VECTOR (3 downto 0);

R5 : in STD\_LOGIC\_VECTOR (3 downto 0);

R6 : in STD\_LOGIC\_VECTOR (3 downto 0);

R7 : in STD\_LOGIC\_VECTOR (3 downto 0);

S : in STD\_LOGIC\_VECTOR (2 downto 0);

Q : out STD\_LOGIC\_VECTOR (3 downto 0));

end component;

component Add\_Sub\_Unit

Port ( A : in STD\_LOGIC\_VECTOR (3 downto 0);

B : in STD\_LOGIC\_VECTOR (3 downto 0);

Sel : in STD\_LOGIC;

S : out STD\_LOGIC\_VECTOR (3 downto 0);



```
C_Out : out STD_LOGIC;  
Z_Out : out STD_LOGIC;  
N_Out : out STD_LOGIC;  
P_Out : out STD_LOGIC );
```

```
end component;
```

```
component MUX_2_way_4_Bit is
```

```
Port ( Adder_Sub_Out : in STD_LOGIC_VECTOR (3 downto 0);  
      lmd_Value : in STD_LOGIC_VECTOR (3 downto 0);  
      S : in STD_LOGIC;  
      Q : out STD_LOGIC_VECTOR (3 downto 0));
```

```
end component;
```

```
component Instuction_Decoder
```

```
Port ( Instruction : in STD_LOGIC_VECTOR (11 downto 0);  
      Reg_en : out STD_LOGIC_VECTOR (2 downto 0);  
      Load_sel : out STD_LOGIC;  
      lmd_Val : out STD_LOGIC_VECTOR (3 downto 0);  
      Reg_SelA : out STD_LOGIC_VECTOR (2 downto 0);  
      Reg_SelB : out STD_LOGIC_VECTOR (2 downto 0);  
      Add_SubSel : out STD_LOGIC;  
      Jump_add : out STD_LOGIC_VECTOR (2 downto 0);  
      Jump_flag : out STD_LOGIC;  
      Reg_Check_Jmp : in STD_LOGIC_VECTOR (3 downto 0));
```

```
end component;
```

```
component Program_Rom is
```

```
Port ( address : in STD_LOGIC_VECTOR (2 downto 0);  
      data : out STD_LOGIC_VECTOR (11 downto 0));
```

```
end component;
```

component Program\_Counter

Port ( D : in STD\_LOGIC\_VECTOR (2 downto 0);

En : in STD\_LOGIC;

Reset : in STD\_LOGIC;

Clk : in STD\_LOGIC;

Q : out STD\_LOGIC\_VECTOR (2 downto 0));

end component;

component Adder\_3\_Bit

Port ( A : in STD\_LOGIC\_VECTOR (2 downto 0);

C\_in : in STD\_LOGIC;

S : out STD\_LOGIC\_VECTOR (2 downto 0);

C\_out : out STD\_LOGIC);

end component;

component MUX\_2\_way\_3\_Bit

Port ( I0 : in STD\_LOGIC\_VECTOR (2 downto 0);

I1 : in STD\_LOGIC\_VECTOR (2 downto 0);

S : in STD\_LOGIC;

Q : out STD\_LOGIC\_VECTOR (2 downto 0));

end component;

signal Imd\_Val\_Ins\_to\_Mux, RCA\_out, Reg\_Check\_Jmp, Add\_Sub\_Out, Data\_Mux\_to\_Reg\_Bank,  
Data\_bus0, Data\_bus1, Data\_bus2, Data\_bus3, Data\_bus4, Data\_bus5, Data\_bus6, Data\_bus7:  
STD\_LOGIC\_VECTOR(3 downto 0);

signal Ins\_Bus : STD\_LOGIC\_VECTOR(11 downto 0);

signal Reg\_bus, Mem\_Bus, Reg\_SelA , Reg\_SelB, Count\_Mux\_to\_PC, Mem\_RCA3\_to\_Mux, Jmp\_Add:  
STD\_LOGIC\_VECTOR (2 downto 0);

signal Add\_Sub\_Sel, Load\_Select\_Ins\_to\_Mux, C\_out\_RCA\_3, Jmp\_Flag: STD\_LOGIC;

```
signal Slow_Clk_Signal: STD_LOGIC;
```

```
signal Mux_A_out , Mux_B_out :std_logic_vector(3 downto 0);
```

```
signal carry_Flag, zero_Flag, negative_Flag, parity_Flag : std_logic;
```

```
begin
```

```
LUT_16_7_0 : LUT_16_7
```

```
port map(
```

```
address => Data_bus7,
```

```
data => seg7_out);
```

```
Slow_Clk_0 : Slow_Clk
```

```
port map (
```

```
    Clk_in => Clk,
```

```
    Clk_out => Slow_Clk_Signal);
```

```
Program_Rom_0 :Program_Rom
```

```
port map (
```

```
address => Mem_Bus,
```

```
data => Ins_Bus);
```

```
Program_Counter_0 : Program_Counter
```

```
port map (
```

```
    D => Count_Mux_to_PC,
```

```
    EN => '1',
```

```
    Reset => Reset,
```

```
    Clk => Slow_Clk_Signal,
```

```
    Q => Mem_Bus);
```

```
Instuction_Decoder_0 : Instuction_Decoder
```

```

port map (
    Instruction => Ins_Bus,
    Reg_en => Reg_bus,
    Load_sel => Load_Select_Ins_to_Mux,
    lmd_Val => lmd_Val_Ins_to_Mux,
    Reg_SelA => Reg_SelA,
    Reg_SelB => Reg_SelB,
    Add_SubSel => Add_Sub_Sel,
    Jump_add => Jmp_Add,
    Jump_flag => Jmp_Flag,
    Reg_Check_Jmp => Reg_Check_Jmp);

```

```

Reg_Check_Jmp <= Mux_A_out;

```

Reg\_Bank\_0 : Register\_Bank

```

port map (
    Reg_en => Reg_bus,
    Clk => Slow_Clk_Signal,
    Reset => Reset,
    Inp => Data_Mux_to_Reg_Bank,
    Q0 => Data_bus0,
    Q1 => Data_bus1,
    Q2 => Data_bus2,
    Q3 => Data_bus3,
    Q4 => Data_bus4,
    Q5 => Data_bus5,
    Q6 => Data_bus6,
    Q7 => Data_bus7 );

```

Add\_Sub\_Unit\_0 : Add\_Sub\_Unit

```

port map( A => Mux_A_out,
    B => Mux_B_out,

```

```
Sel => Add_Sub_Sel,  
S => Add_Sub_Out,  
C_Out => carry_Flag,  
Z_Out => zero_Flag,  
N_Out => negative_Flag,  
P_Out => parity_Flag );
```

Mux\_2\_way\_4\_Bit\_0 : Mux\_2\_way\_4\_Bit

```
port map (  
  S => Load_Select_Ins_to_Mux,  
  Adder_Sub_Out => Add_Sub_Out,  
  Imd_Value => Imd_Val_Ins_to_Mux,  
  Q => Data_Mux_to_Reg_Bank);
```

MUX\_8\_way\_4\_Bit\_A : MUX\_8\_way\_4\_Bit

```
port map (  
  R0 => Data_bus0,  
  R1 => Data_bus1,  
  R2 => Data_bus2,  
  R3 => Data_bus3,  
  R4 => Data_bus4,  
  R5 => Data_bus5,  
  R6 => Data_bus6,  
  R7 => Data_bus7,  
  S => Reg_SelA,  
  Q => Mux_A_out );
```

MUX\_8\_way\_4\_Bit\_B : MUX\_8\_way\_4\_Bit

```
port map (  
  R0 => Data_bus0,
```

```
R1 => Data_bus1,  
R2 => Data_bus2,  
R3 => Data_bus3,  
R4 => Data_bus4,  
R5 => Data_bus5,  
R6 => Data_bus6,  
R7 => Data_bus7,  
S => Reg_SelB,  
Q => Mux_B_out );
```

Adder\_3\_Bit\_0 : Adder\_3\_Bit

port map (

```
A => Mem_Bus,  
C_in => '0',  
S => Mem_RCA3_to_Mux,  
C_out => C_out_RCA_3);
```

MUX\_2\_way\_3\_Bit\_0 : MUX\_2\_way\_3\_Bit

port map (

```
S => Jmp_Flag,  
I0 => Mem_RCA3_to_Mux,  
I1 => Jmp_Add,  
Q => Count_Mux_to_PC);
```

Overflow <= carry\_Flag;

Zero <= zero\_Flag;


R7 <= Data\_bus7;

anode <= "1110";


end Behavioral;

Timing Diagrams


Instruction Decoder

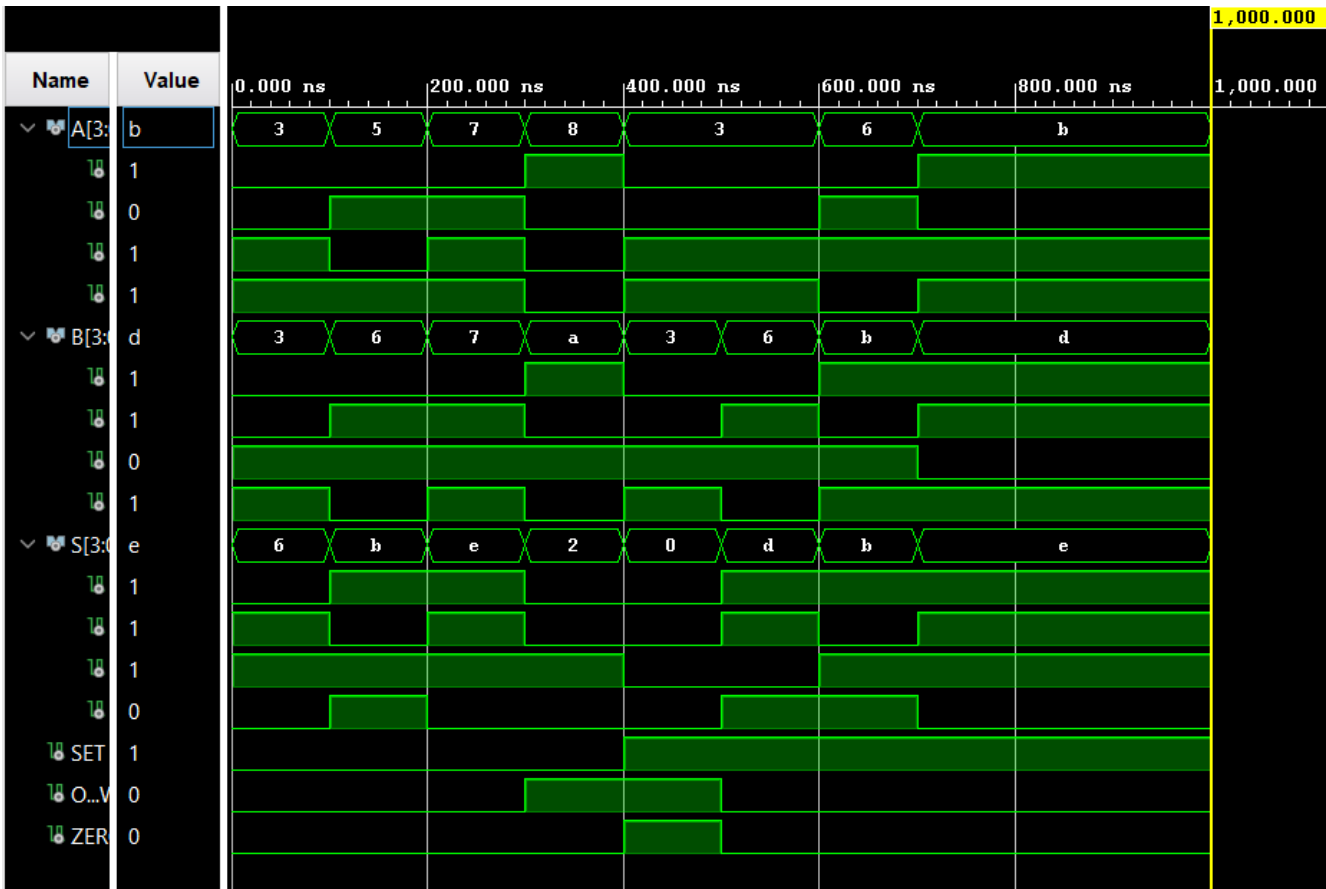


3 bit Adder

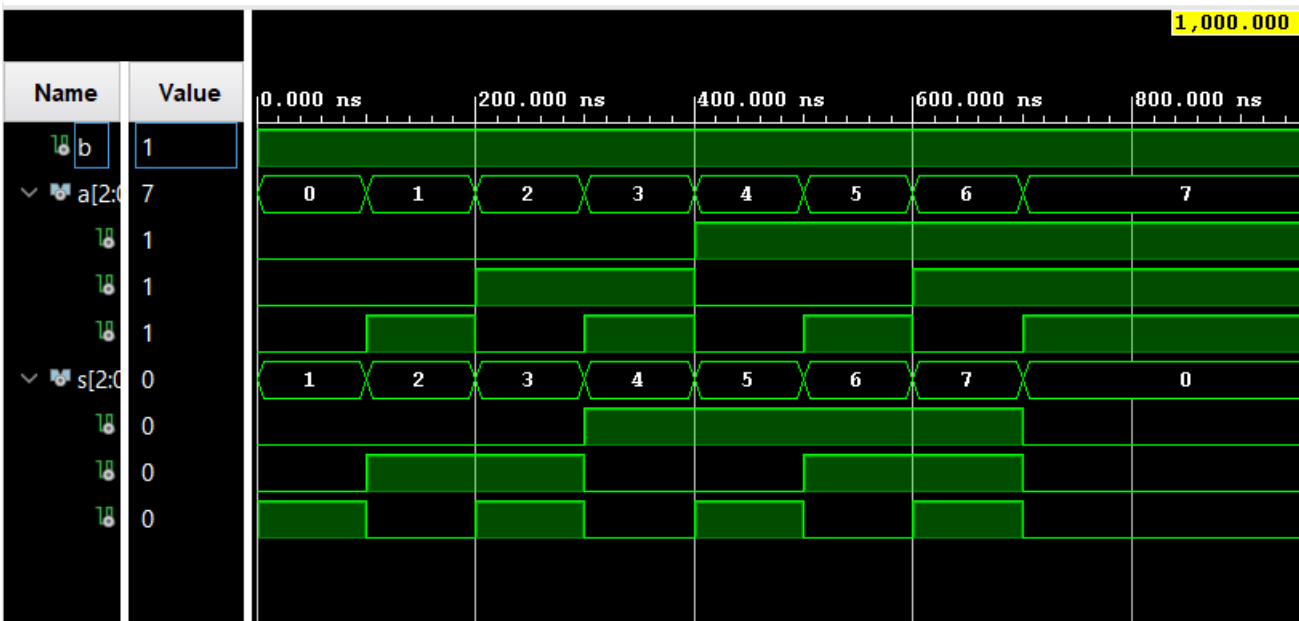



Adder Substraction Unit

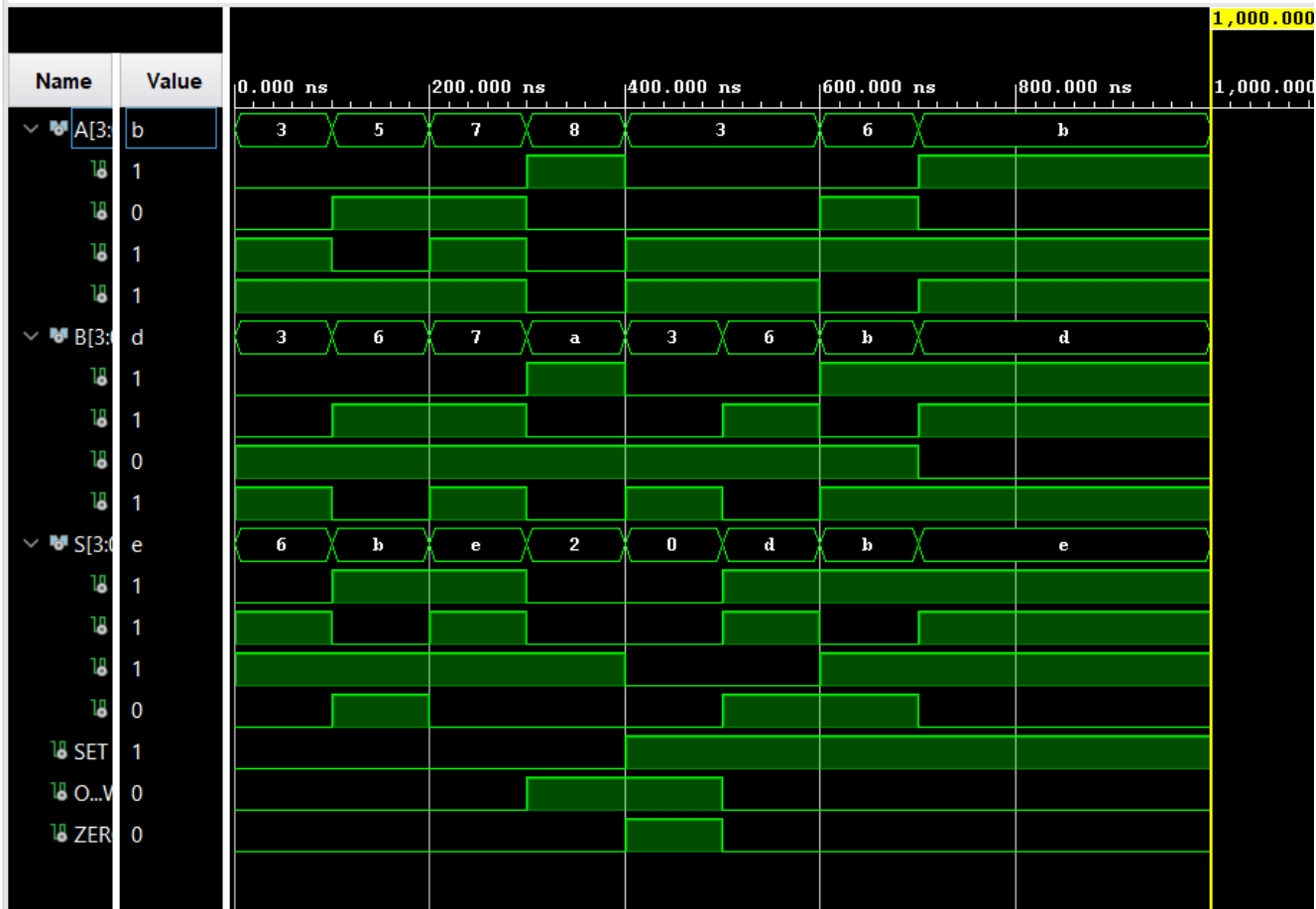


Register bank

 




  


Program Rom

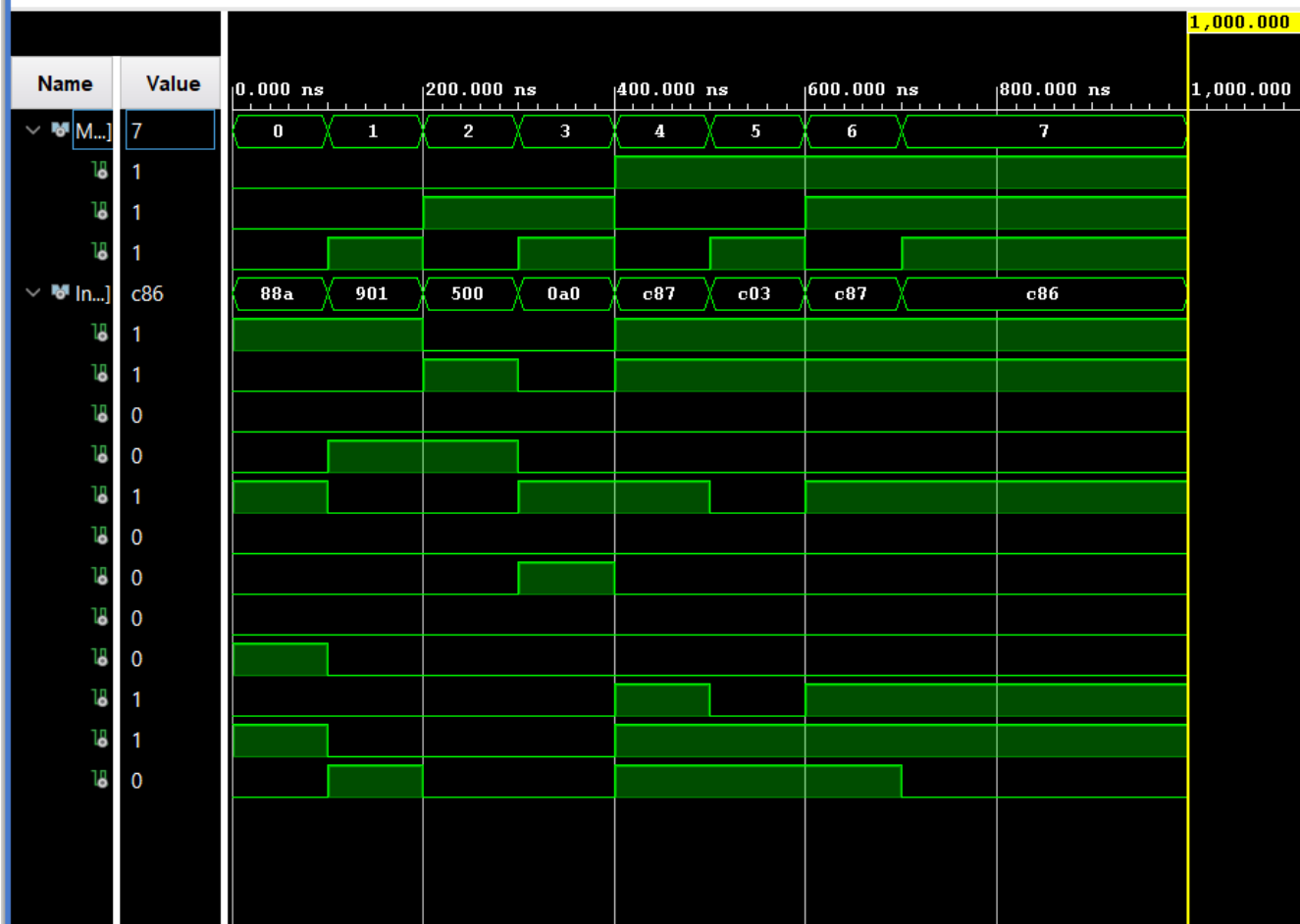

Program Counter

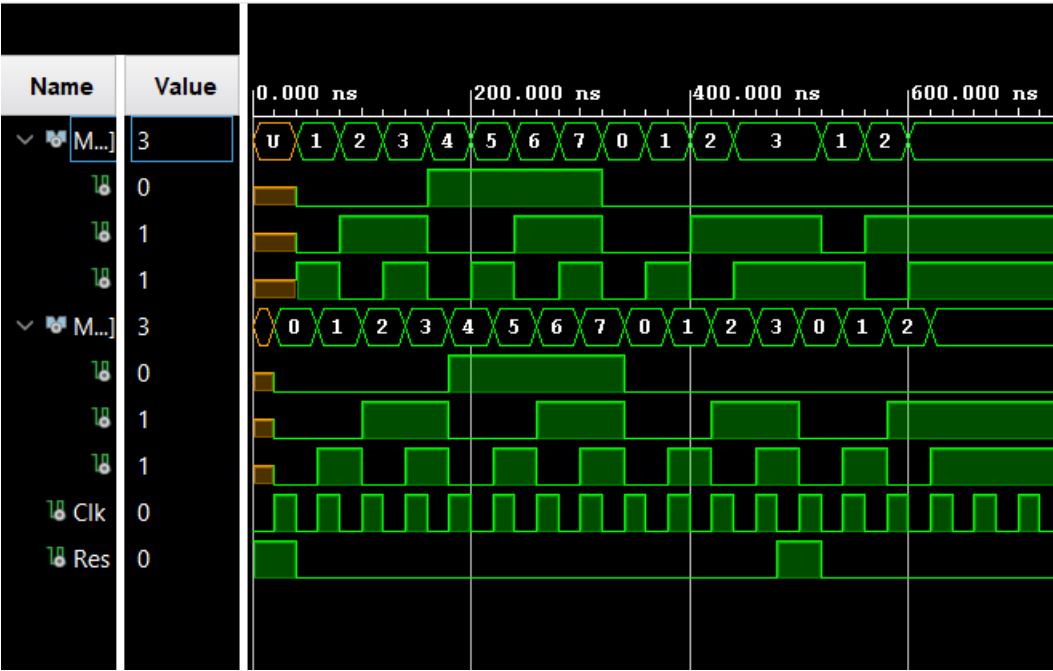

## Nano Processor

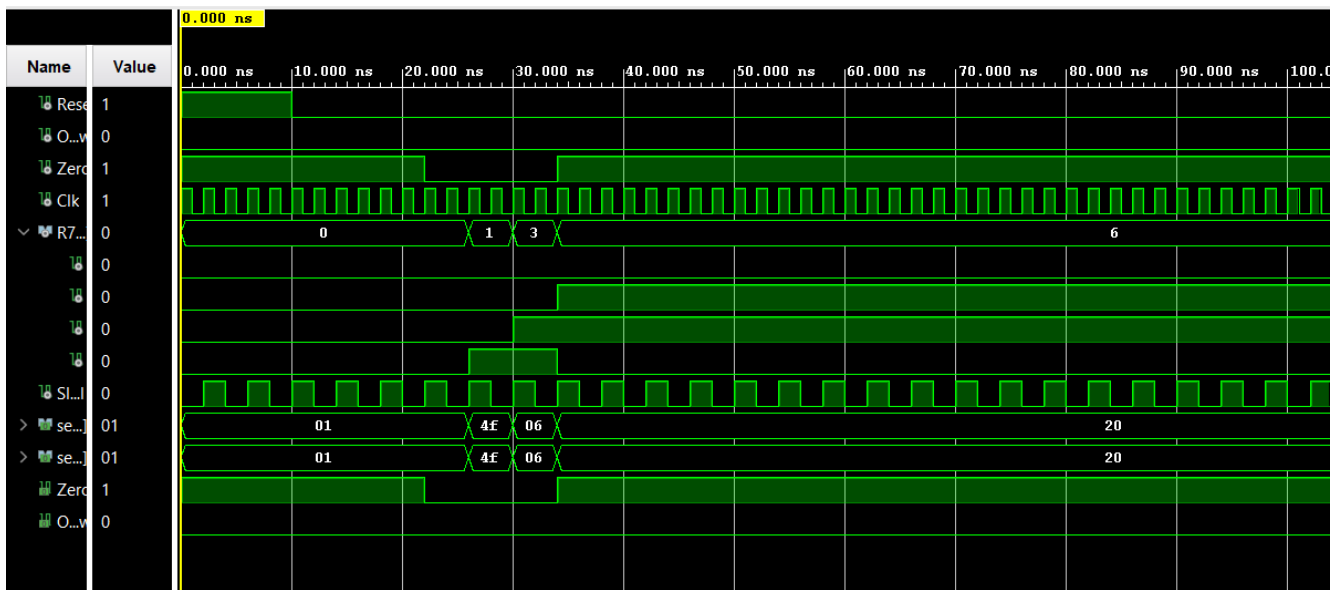

## Conclusion

- Learnt to develop a functional nano-processor that could execute simple assembly instructions like ADD, MOV, NEG and JNZ and display the output value on a seven segment display.
- In addition we were able to further optimize the design by using a behavioral approach to design the MUXs instead of decoders.
- Understood the importance of simulation of the circuits before programming on the boards.

**Contribution:** We totally spent 6 hours each and shared the work among us.

Kopimenan	Instruction Decoder, Program Counter, Program ROM, Register Bank
Sajeev	Adder Substraction Unit, Muxes, 3 bit Adder